

Charge/Current/Voltage


Charge
 $q_e = -1.602 \times 10^{-19} \text{ C}$
 $q_p = 1.602 \times 10^{-19} \text{ C}$
 q
 - measured in Coulombs (C)
 $q = \int_{t_1}^{t_2} i dt$

Current

i
 - measured in A, C/s
 ampere = C/s

Voltage

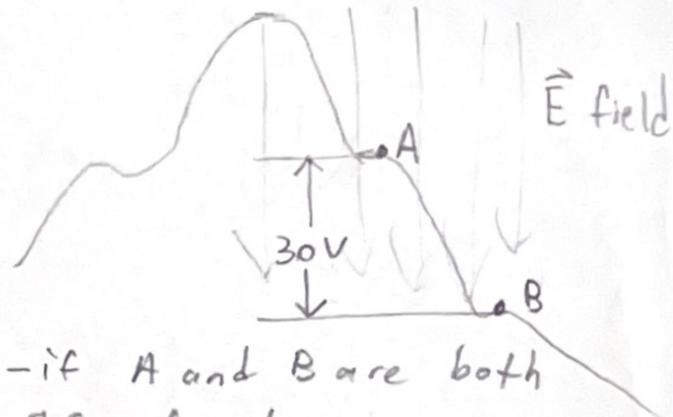V
 - measured in Volts
 - Electric height
 Volt = J/C



- if A and B are both IC of charge
 - A → B, delivers 30J of energy
 - B → A, costs 30J of energy

Average Current

$q(t)$
 - How many net C of charge have passed the checkpoint to the right at a given time

$-i_{avg} = \frac{\Delta q}{\Delta t}$

Instantaneous Current

$i(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t}$
 $i = \frac{dq}{dt}$

Energy

W
 - measured in Joules
 $W = \int_{t_1}^{t_2} V i dt$

Power


P
 - measured in Watts
 Watt = J/s
 $P = Vi$

$P = \frac{dW}{dt}$; $t = \frac{W}{Vi}$
 $W = \int_{t_1}^{t_2} p dt$

Current flowing:
 uphill → Delivering power
 downhill → absorbing power

Tellegens Theorem

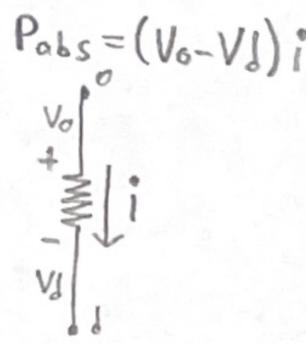$\sum P_{abs} - \sum P_{del} = 0$
 - Total absorbed power equals total delivered power in a circuit



Circuits

Branch

- a link between two proper nodes
 - may have zero or more binary nodes

Binary Node

- Does not affect the shape of the circuit


Atomic Branch

- Branch with no binary nodes

Branch

- The path that joins two true nodes. Atomic if no binary nodes inside

Binary Node

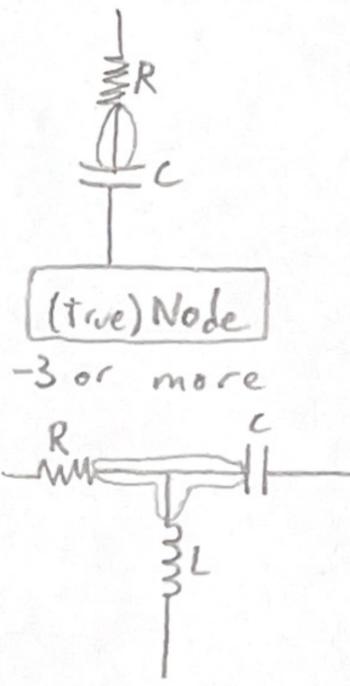

Series

- Elements in the same branch are in series

Parallel

- ① Both elements are in atomic branches
- ② Both atomic branches share the same true nodes. Must share both

Series/Parallel

- Two elements in series have the same current. But two elements that have the same current aren't necessarily in series
- Two elements in parallel have the same voltage but not the other way

Circuit with no true nodes

- Promote one B-node to rank of true node (arbitrary)

Active Element

Battery, generator, etc., sources
 Deliver power (usually)

Passive Element

Resistor, inductor, capacitor
 Absorb power (sometimes)

Resistance

- resists currents i

Inductance

- resists changes in currents $\frac{di}{dt}$

Capacitance

- Resists changes in voltages $\frac{dV}{dt}$

Passive element

- Assume water falls from the sky

Ohm's Law - R in Ohms (Ω)



$$\Omega = V/A$$

- ① Resistance
- ② Power rating

Inductor - L in Henrys

Henry (H)

$$V = L \frac{di}{dt}$$

- ① Inductance
- ② Current rating

Capacitor

- C in Farads (F)



$$i = C \frac{dV}{dt}; V = \frac{q}{C}$$

- ① Capacitance
- ② Voltage rating

Active (Sources)

Dependent:

Independent:

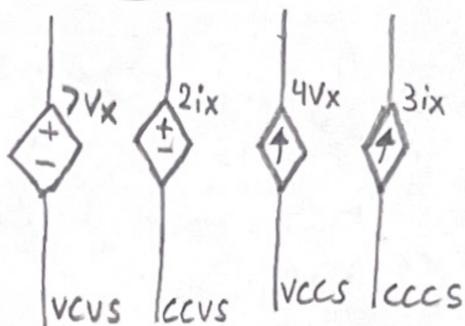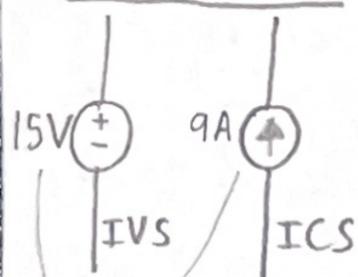

Kirchoff's Current Law

$$\sum_{\text{node}} i_{in} = \sum_{\text{node}} i_{out}$$

$$\sum_{\text{Gauss}} i_{in} = \sum_{\text{Gauss}} i_{out}$$

$$\sum_{\text{Bdry}} i_{in} = \sum_{\text{Bdry}} i_{out}$$

Inverses

Conductance:

$$G = \frac{1}{R} \text{ - measured in Siemens}$$

Inductance⁻¹:

$$\Gamma = \frac{1}{L} \text{ - measured in H}^{-1}$$

→ gamma

Capacitance⁻¹:

$$T = \frac{1}{C} \text{ - measured in F}^{-1}$$

Kirchoff's Voltage Law


- a loop is a closed path that only crosses a node once, ie: arrive in it and leave out of it

Window pane (Mesh)

- a loop that does not contain any loops inside

Neither in Series/Parallel

Triangle/Delta/Pi Config:

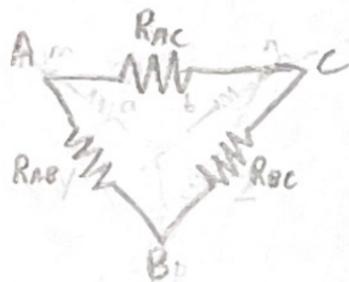

-Delta to Wye (Y):

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_D = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_E = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_F = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$


$$R_G = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$G_x = \frac{G_x G_y}{G_x + G_y + G_z}$$

$$G_y = \frac{G_b G_c}{G_a + G_b + G_c}$$

$$G_z = \frac{G_c G_a}{G_a + G_b + G_c}$$

Star/Wye/tee config:

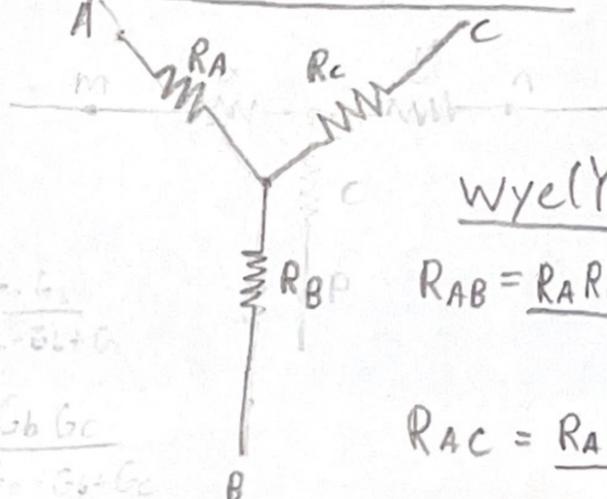

Wye (Y) to Delta:

$$R_{AB} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_C}$$

$$R_{AC} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_B}$$

$$R_{BC} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_A}$$

Addition Simplification

$$R_{eq} = R_1 + R_2 + \dots + R_n \text{ SERIES}$$

$$L_{eq} = L_1 + L_2 + \dots + L_n \text{ SERIES}$$

$$V_{source} = V_1 + V_2 + \dots + V_n \text{ SERIES}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n \text{ PARALLEL}$$

$$I_{source} = i_1 + i_2 + \dots + i_n \text{ PARALLEL}$$

Inverse Simplification


$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)^{-1} \text{ PARALLEL}$$

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)^{-1} \text{ PARALLEL}$$

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)^{-1} \text{ SERIES}$$

*midterm demonstrate not on slides


Source Transformations

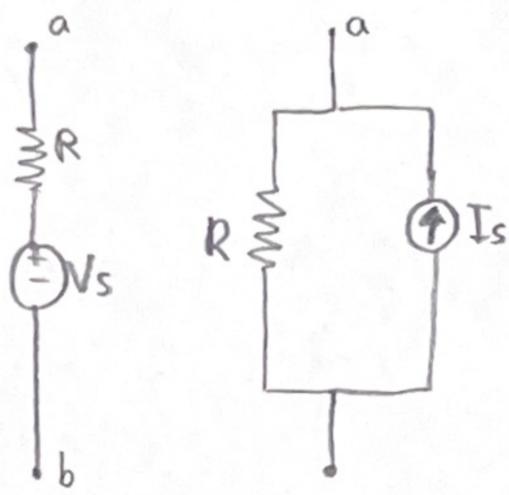

$$V_s = R I_s$$

$$I_s = \frac{V_s}{R}$$

Voltage Divider

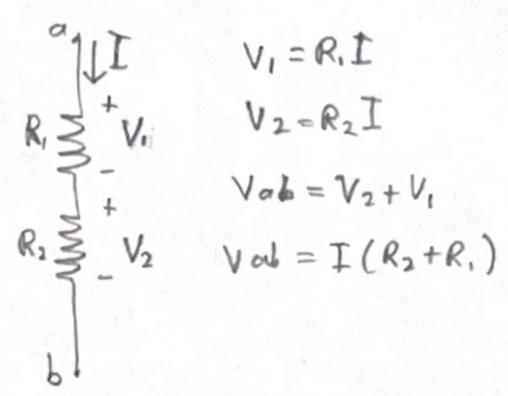

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$


$$V_{ab} = V_2 + V_1$$

$$V_{ab} = I(R_2 + R_1)$$


$$\frac{V_1}{V_{ab}} = \frac{R_1}{R_{eq}} \quad \text{"Same \%"}$$

Superposition

killing a V source: killing a I source:

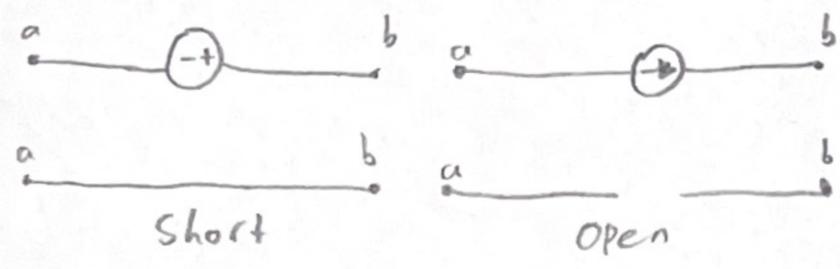

Current Divider

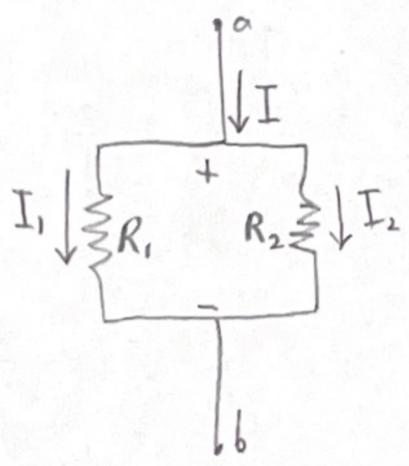

$$I_1 = \frac{V_{ab}}{R_1}$$

$$I_2 = \frac{V_{ab}}{R_2}$$


$$I = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_{ab}$$

$$\frac{I_1}{I} = \frac{R_2}{R_1 + R_2} \quad \text{"Same \%"}$$


$$\frac{I_1}{I} = \frac{G_1}{G_1 + G_2}$$

Modified Nodal Analysis


Controlling Variable:

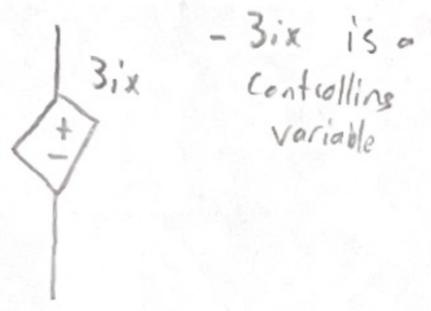

Evil currents:

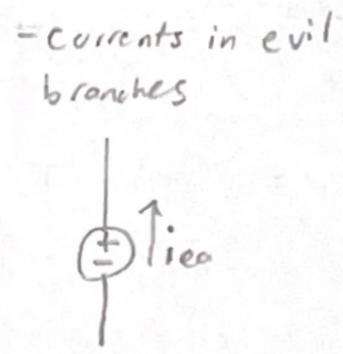

Thevenin and Norton Equivalents

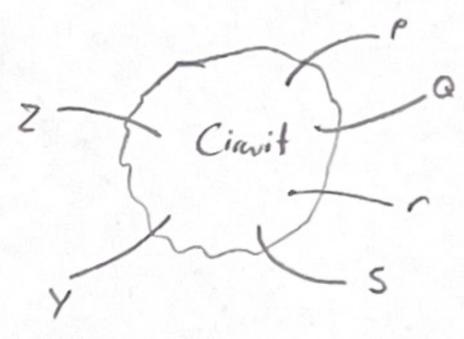


Two nodes = one part
(could be binary or true)


Solution Method

- ① Choose REF node
- ② Choose R/RV current directions
- ③ Label every true node (KCL)
- ④ Label every evil current (EVL)
- ⑤ Label every controlling variable (CTL)

(4) New ideal Circuit Elements

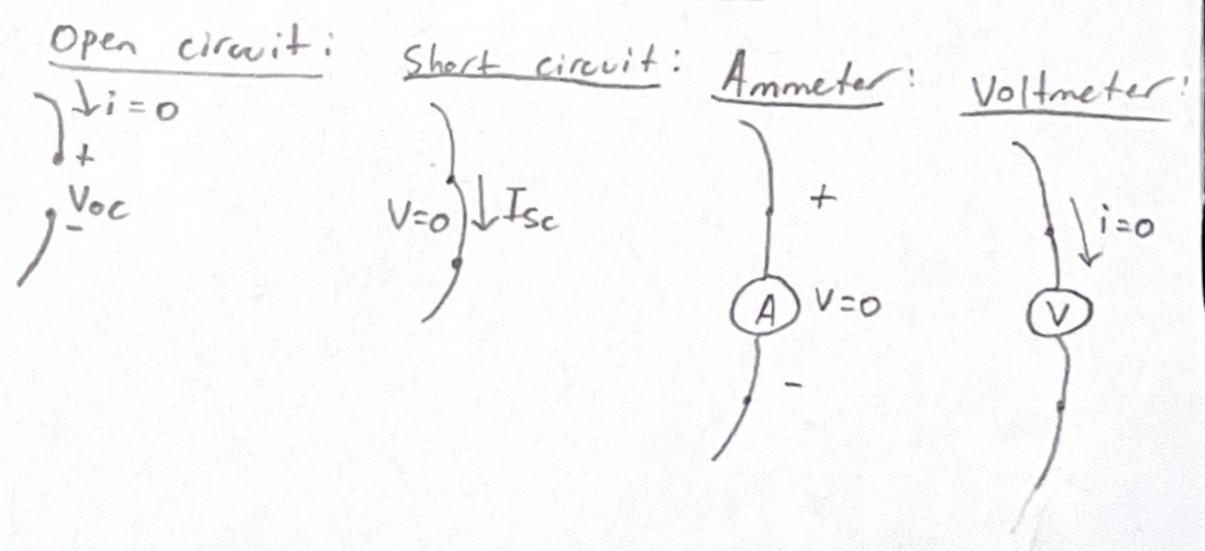


Classic Method

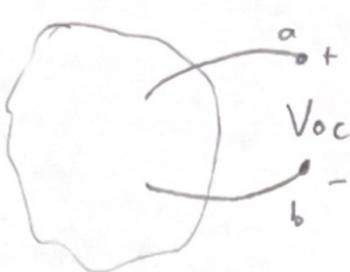

$V_{TH} = V_{oc}$

Open circuit test:

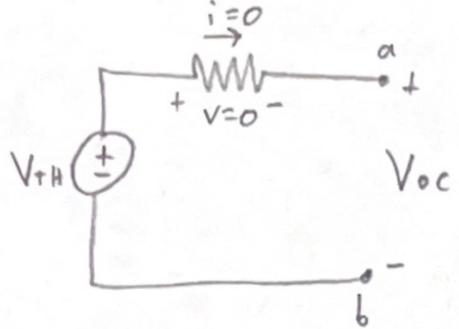


$I_{sc} = \frac{V_{TH}}{R_{TH}}$

$R_{TH} = \frac{V_{TH}}{I_{sc}}$

R_{TH}

short circuit test:

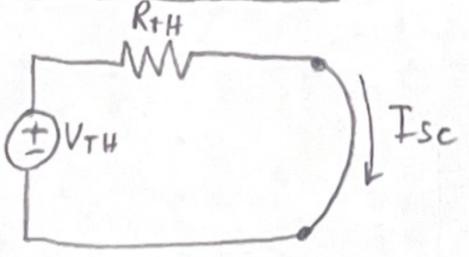


Kill Sources (All independent)

- Find $R_{eq} = R_{TH}$


only controlled sources

$V_{oc} = 0$

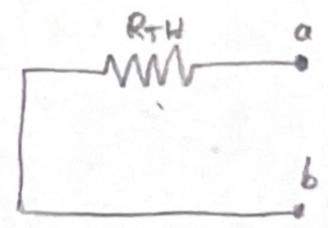


How....:

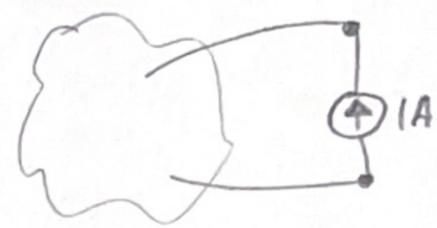apply a 1Amp current between the nodes, solve for R_{TH}




Norton Mayer Equivilant

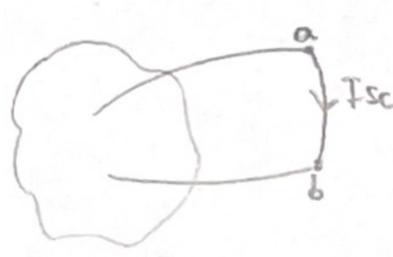


$I_N = I_{sc}$

short circuit test:

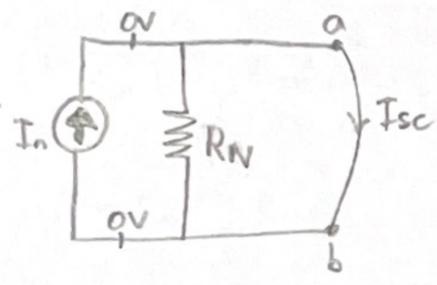

open circuit test:

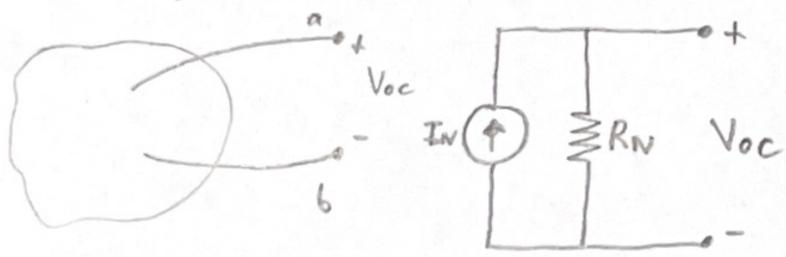



$V_{oc} = R_N I_N$

$R_N = \frac{V_{oc}}{I_N}$

$R_N = \frac{V_{oc}}{I_{sc}}$

Two Resistors Method

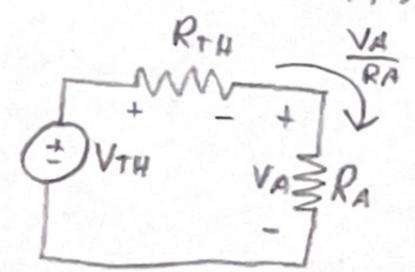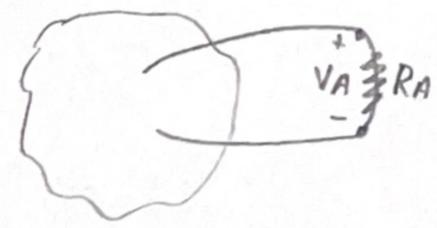"In real life its dangerous to apply short circuit test"




"Do this again with a second Resistor Re"

SOLVE for V_{TH}, R_{TH}

$V_{TH} - R_{TH} \frac{V_A}{R_A} = V_A$

$V_{TH} - R_{TH} \frac{V_B}{R_B} = V_B$

1 and 2A (UBC) Method

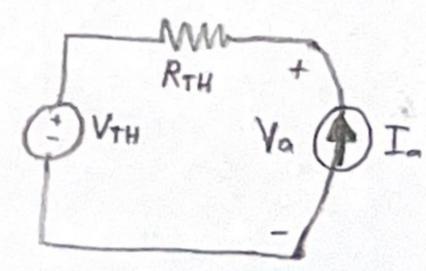

$V_{th} + R_{th} I_a - V_a = 0$

$V_{th} + R_{th} I_b - V_b = 0$

"Repeat with new source"


Max Power Criterion

$P_{MAX} = \frac{V_{th}^2}{4R_{th}}$

$P_{MAX} = \frac{I_{sc}^2 R_{th}}{4}$

First order Circuits


RL Circuit

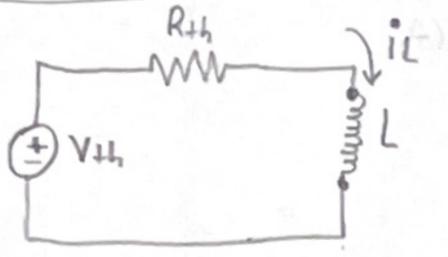

DE: $L \frac{di_L}{dt} + R i_L = V_s = 0$

Sol'n: $i_L(t) = (I_0 - \frac{V_s}{R}) e^{-t/(L/R)} + \frac{V_s}{R}$

RC Circuit

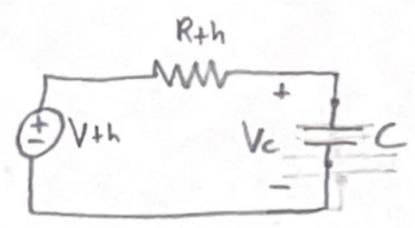

DE: $RC \frac{dV_c}{dt} + V_c = V_{th}$

Sol'n: $V_c(t) = (V_{c0} - V_{th}) e^{-t/RC} + V_{th}$


Impedance

$Z_L = Lp$ * $p = \frac{d}{dt}$
 $Z_C = \frac{1}{Cp}$ (s^{-1})
 $Z_R = R$


General Ohm's Law:

$V = Z \cdot i$
 Volts / impedance = Current

R/L/C Impedance

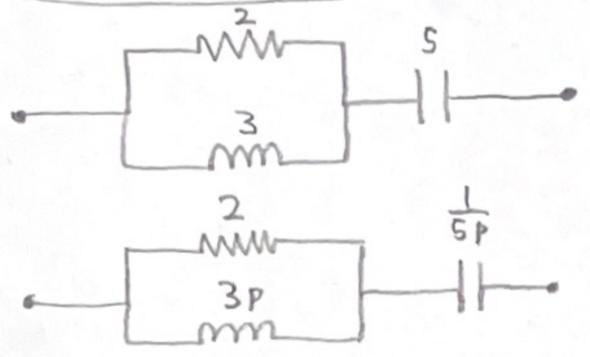

Right after we move a switch $t=0^+$

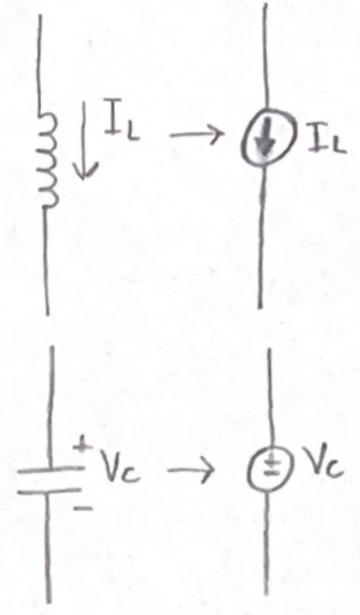


Capacitor

where V_0 is initial voltage
 $V_c = V_0 e^{-t/RC}$
 $Q = C V_0 e^{-t/RC}$
 $I = \frac{V_0}{R+L} e^{-t/RC}$

Inductor


where V_b is final voltage
 $V_L = V_b e^{-t/R/L}$
 $I = \frac{V_b}{R} (1 - e^{-t/R/L})$

Operational Amplifiers

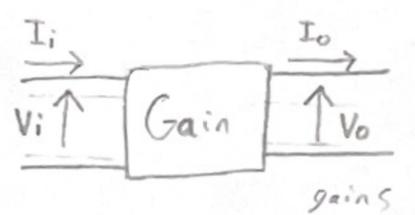

$A_v = \frac{V_o}{V_i}$ (V/V) $A_I = \frac{I_o}{I_i}$ (A/A) $A_p = \frac{P_o}{P_i}$ (W/W)

$A_v^{dB} = 20 \log_{10} \left| \frac{V_o}{V_i} \right|$ $A_I^{dB} = 20 \log_{10} \left| \frac{I_o}{I_i} \right|$ $A_p^{dB} = 10 \log_{10} \left| \frac{P_o}{P_i} \right|$

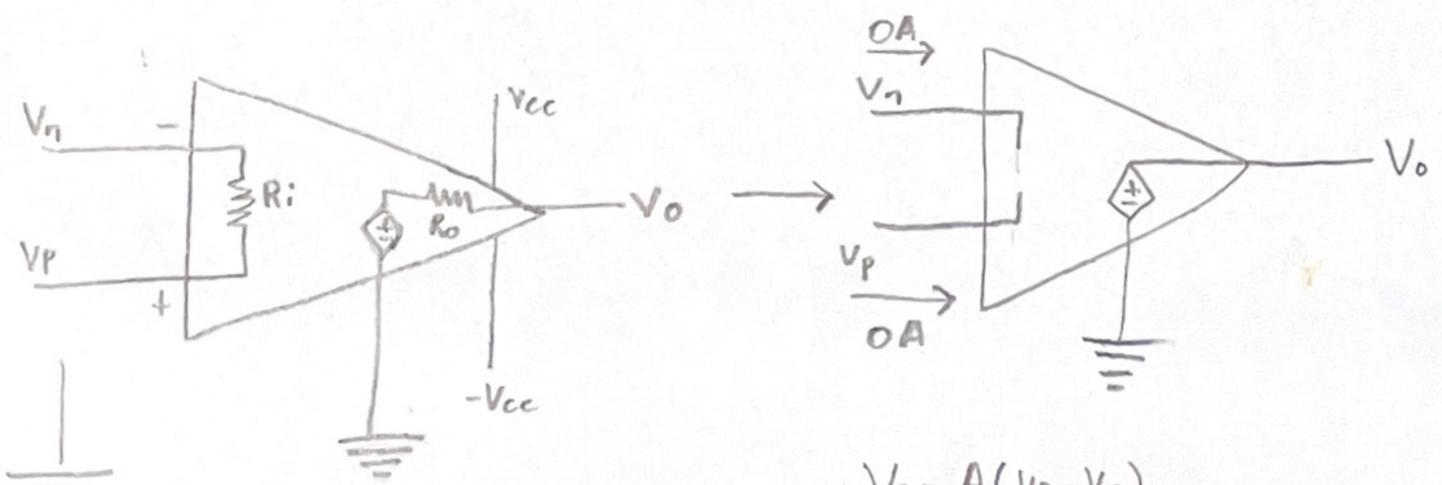


$V_o = A(V_p - V_n)$

$R_i = \infty$
 $R_o = 0$
 $A = \infty$ (voltage gain)

$V_c(t) = (V_{c0} - V_{cf}) e^{-t/RC} + V_{cf}$
 $I_L(t) = (I_{L0} - I_{Lf}) e^{-t/R/L} + I_{Lf}$
 where V_{c0} and I_{L0} are DCSS of both
 $V_{cf} = V_{th}$ seen by capacitor
 $I_{Lf} = I_{th}$ seen by inductor

Negative Feedback

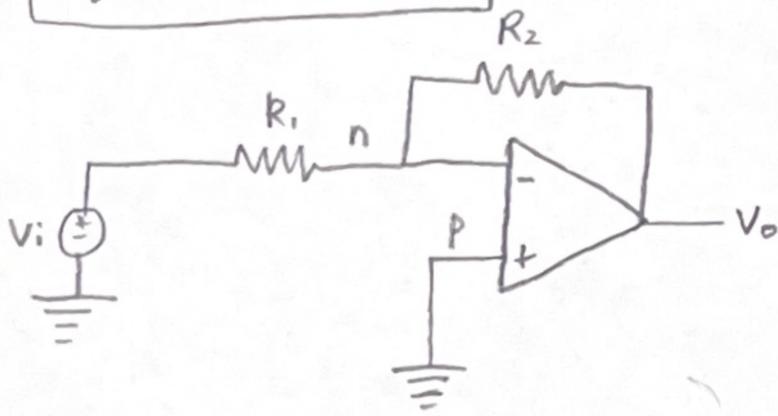

-connecting the output to the inverting input by passive elements

Inverting amplifier


$V_p = V_n$
 $V_p = 0$ - Don't write a kel for V_o

$V_p = V_n$
 -as long as no saturation

$$n: \frac{V_i - V_n}{R_1} = 0 + \frac{V_n - V_o}{R_2}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_i$$


Non-Inverting Amplifier

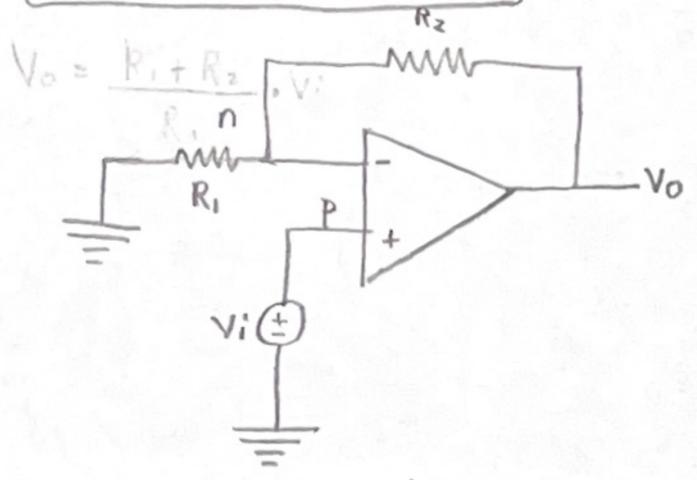

$V_p = V_n$
 $V_p = V_i$
 $\therefore V_o = \frac{R_1 + R_2}{R_1} \cdot V_i$

$$n: \frac{V_o - V_n}{R_2} = 0 + \frac{V_n}{R_1}$$

Ideal Diode

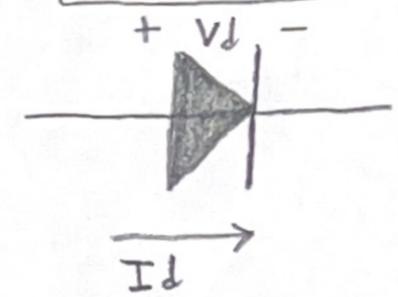

$$I_d = I_o e^{V_D / V_T} \quad \text{Constant}$$

Saturation


$$-V_{cc} \leq V_o \leq +V_{cc}$$

Positive Saturated $\rightarrow V_o = +V_{cc}$
 $V_p > V_n$


Negative Saturated $\rightarrow V_o = -V_{cc}$
 $V_p < V_n$

Diodes

Ideal diode

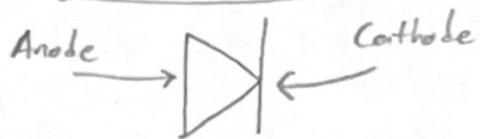

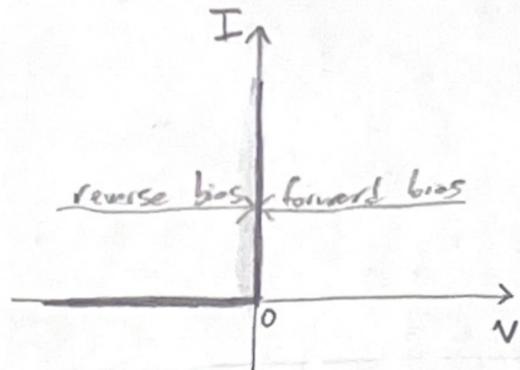- Allows current to flow in one direction
- No voltage drop across terminals when allowing current to flow



Real diode

- Allows a small amount of reverse current
- Has a small voltage drop when current flowing

Ideal Model

- Try all possibilities
- 2ⁿ possibilities where n is the number of diodes

Simplified eqn:

- Because usually $i \gg I_s$, $v \gg 10nV_T$
- $i \approx I_s e^{\frac{v}{nV_T}}$

Models

- 1 Ideal Model
- 2 Exponential Model
- 3 Constant Voltage Drop
- 4 Piecewise linear
- 5 Small signal Model


Small Signal Model

- 1 Solve the operating point of the diode in the DC circuit.

To get DC:


- Short all AC voltage sources
- Open all AC current sources
- Short all inductors
- Open all capacitors

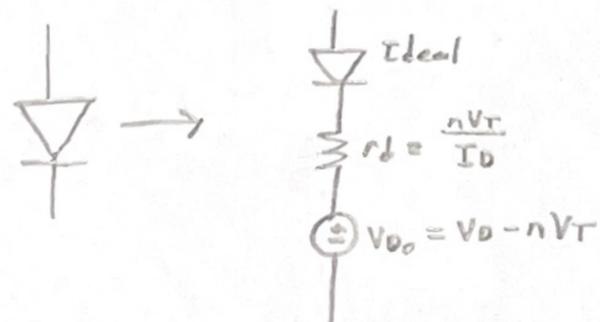- 2 Replace diode with its small signal equivalent in AC circuit



To get AC:

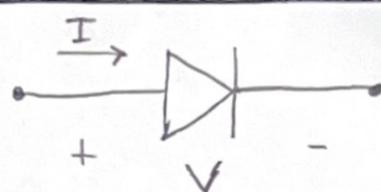- Short all DC voltage sources
- Open all DC current sources
- Open all inductors
- Short all capacitors



(2) modes of operation:

- 1 Reverse bias: $V < 0$, $I = 0$, behaves like open circuit
- 2 Forward bias: $V = 0$, $I > 0$, behaves like short circuit

$$i = I_s (e^{\frac{v}{nV_T}} - 1)$$

where: i = current through the diode
 v = voltage across the diode
 I_s = reverse saturation current, very small usually $10^{-12}A$ or $10^{-15}A$

Equation Model

- Make a system of equations
- Most accurate
- Hard without a calculator
- Also called the exponential model


n = empirical constant
 V_T = Thermal voltage

$$V_T = \frac{kT}{q}$$



where:
 k = Boltzmann's constant
 T = absolute temperature
 q = base charge

Constant Voltage Drop

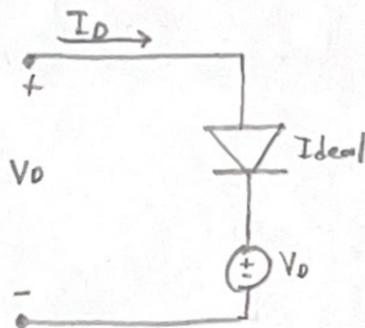- The diode can be replaced with an ideal diode and voltage source in series



Piecewise Linear Model

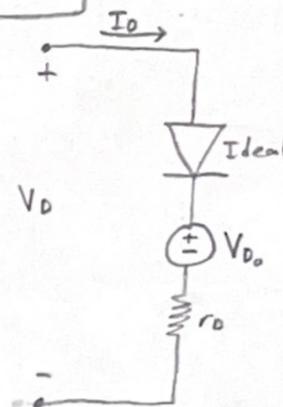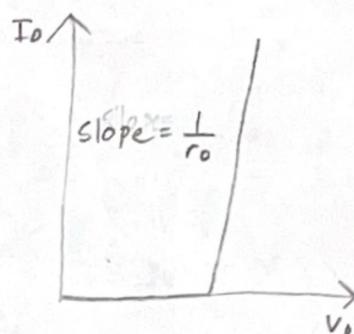


$$\frac{1}{r_D} = \frac{I_{mA} - 0mA}{0.7V - V_{D0}}$$

- To find V_{D0}

Zener diode




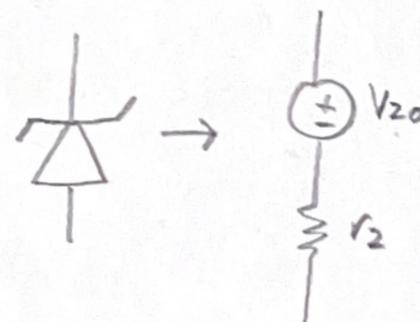- allows current to flow in reverse at certain voltage



$$V_{z0} = V_z - r_z I_z$$


Rectifier Circuits

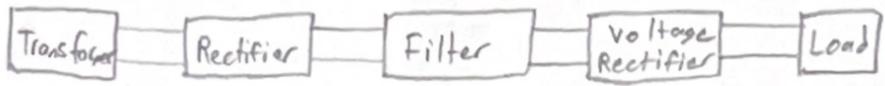

Types of Rectifiers

- ① Half-Wave
- ② Full-Wave:
 - Center tap
 - Bridge type


Half-Wave Rectifier

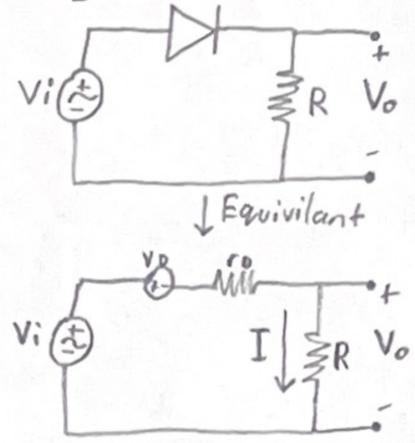


$$I = \frac{V_i - V_o}{R + r_D}$$

$$V_o = R \left(\frac{V_i - V_p}{R + r_D} \right)$$

Full Wave Bridge Rectifier

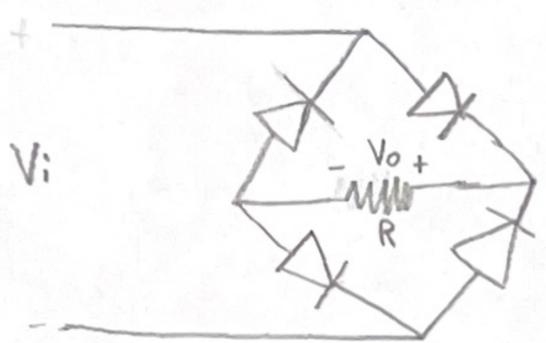


Zener diodes as Shunt Voltage regulators

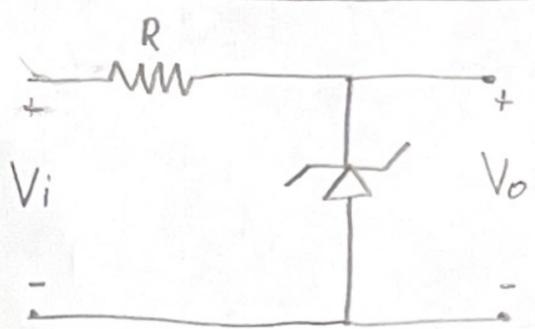

$$\text{Line regulation} = \frac{\Delta V_o}{\Delta V_{in}}$$

$$\text{Load regulation} = \left| \frac{\Delta V_o}{\Delta I_L} \right|$$

Rectifier Circuit with resistive load

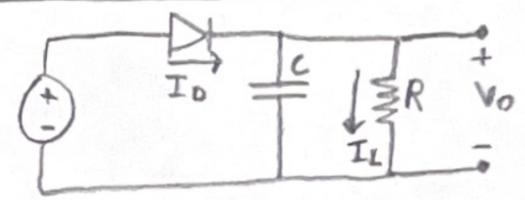

For Half wave:

$$V_r = \frac{V_p T}{RC} = \frac{V_p}{fRC} = \frac{I_L}{fC}$$

For Full wave:

$$V_r = \frac{V_p T}{2RC} = \frac{V_p}{2fRC} = \frac{I_L}{2fC}$$

Load Voltage:

$$V_L = V_p - \frac{1}{2} V_r$$

When ripple is small


$$I_L = \frac{V_p}{R_L}$$

Load Current:


$$I_L = \frac{V_L}{R_L}$$

BJT's

NPN transistor

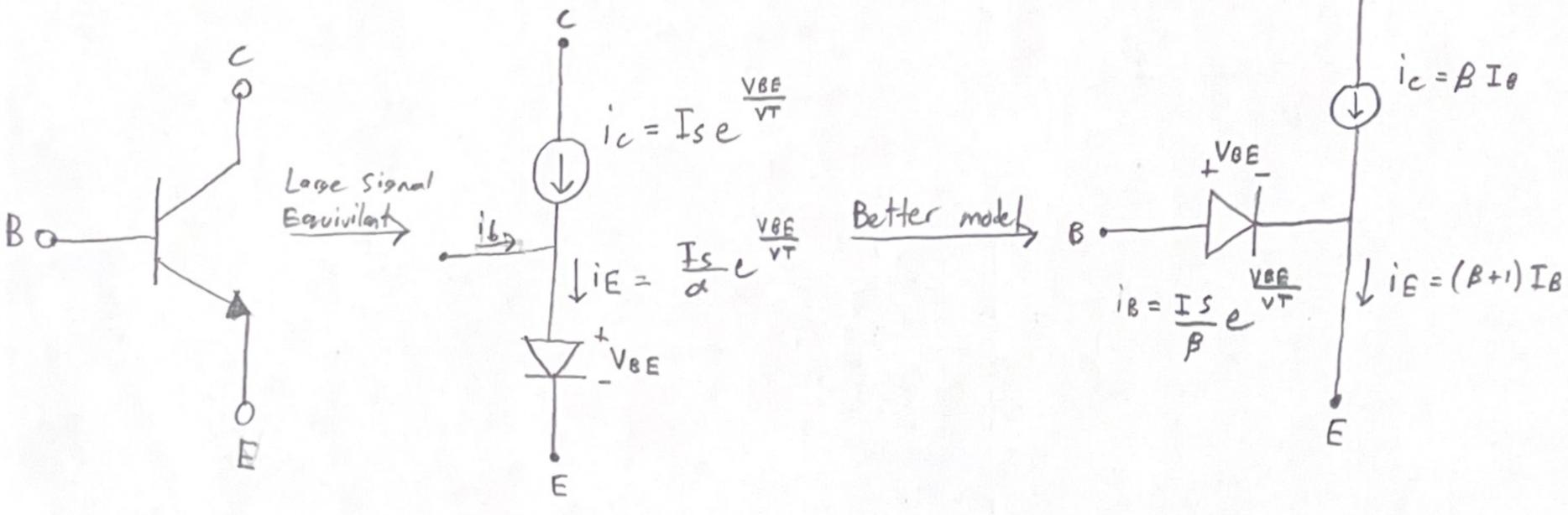


PNP Transistor

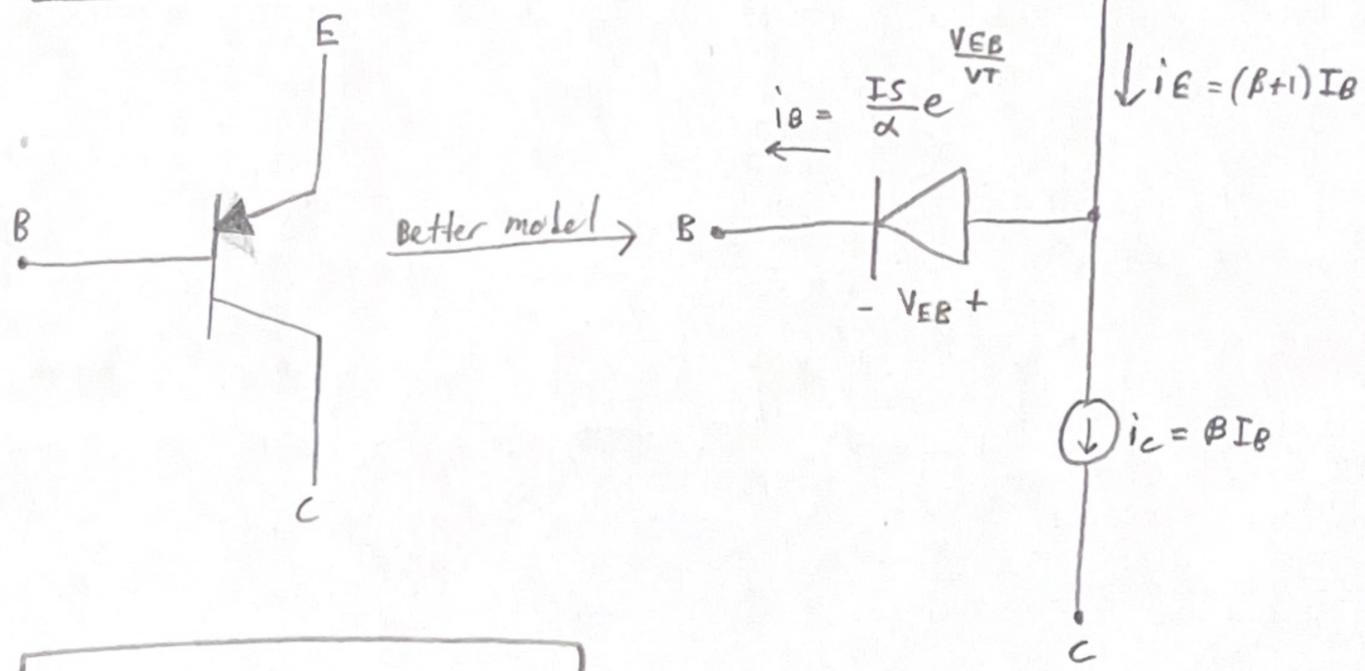

* only work in active region

Modes of Operation

BJT Mode	Collector Current (I_c)
Cutoff	$i_c = 0$
Active	$i_c = \beta \cdot I_B$
Saturation	$i_c < \beta \cdot I_B$

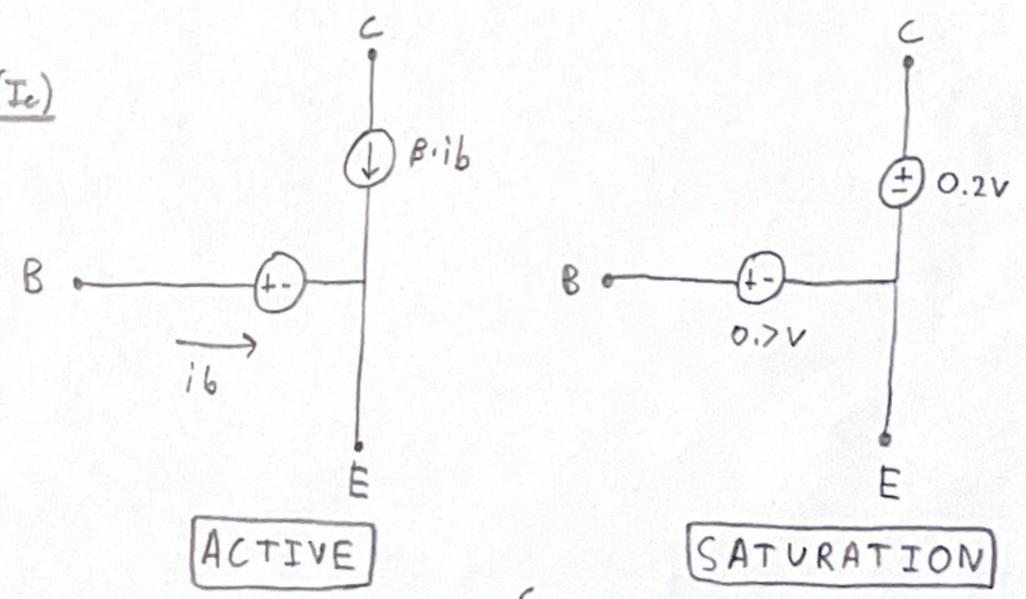


Relationships

$$I_E = I_B + I_C$$

$$I_C = \beta \cdot I_B$$

$$I_C = \alpha \cdot I_E$$
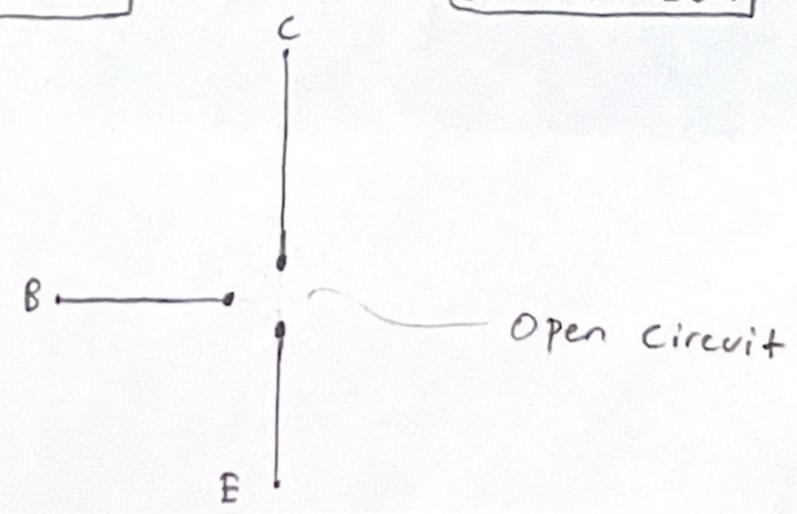
$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha}$$



BJT Amplifiers


Models

$$g_m = \frac{I_c}{V_T}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

Steps:


Hybrid- π model:

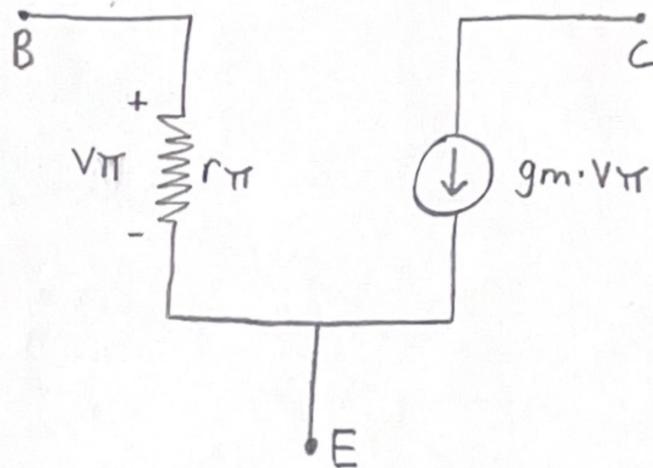

Input Resistance (R_i) → use hybrid- π model if R_i is measured from the base. (use r_{π})

T-model:

$$r_e = \frac{\alpha}{g_m}$$

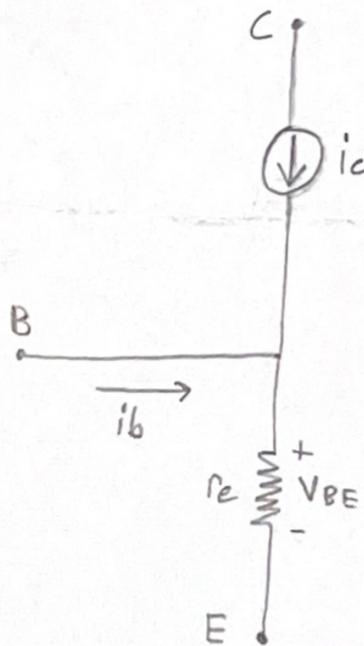

Input Resistance (R_i) → use T-model if R_i is measured from the base. (use r_e)

① Get DC circuit:

- Short all AC $V_{sources}$
- Open all AC $I_{sources}$
- open all capacitors
- short all inductors

② Solve circuit for I_c, r_{π} (or r_e), g_m :

③ Get AC circuit:


- replace transistor with hybrid- π circuit
- Short all DC $V_{sources}$
- open all DC $I_{sources}$
- Short all capacitors
- open all inductors

④ Solve AC circuit for (gain)

Formulas

MOSFETs

Enhancement N-MOSFET

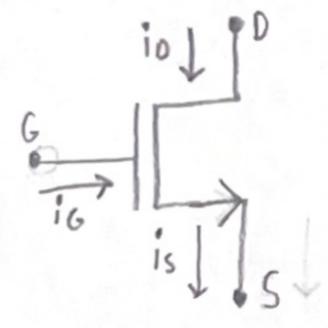

Triode Region $V_{DS} < V_{GS} - V_t$


$$i_D = i_S = k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Saturation Region $V_{DS} > V_{GS} - V_t$

$$i_D = i_S = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

Cutoff Region $V_{GS} < V_t$

$$i_D = 0$$

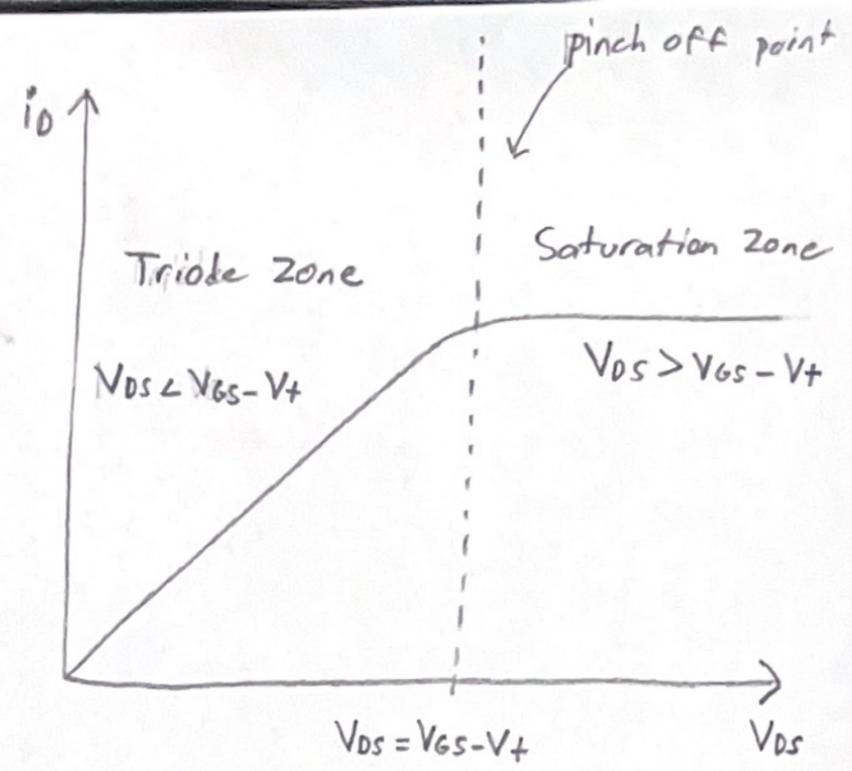

Small V_{DS} Assumption $V_{DS} < 0.2V$


* in Triode Region

$$i_D \approx k_n' \frac{W}{L} [(V_{GS} - V_t) V_{DS}]$$

where: $r_{DS} \approx \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_t)}$

$$r_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)}$$

Enhancement P-MOSFET

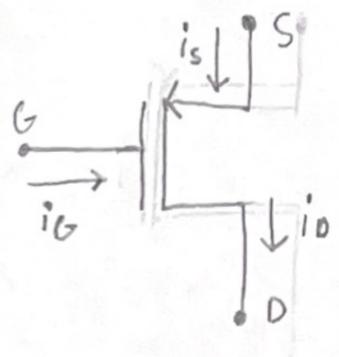

Triode Region $|V_{DS}| < |V_{GS} - V_t|$

$$i_D = i_S = k_p' \frac{W}{L} \left[(|V_{GS} - V_t|) |V_{DS}| - \frac{1}{2} V_{DS}^2 \right]$$

Saturation Region $|V_{DS}| > |V_{GS} - V_t|$

$$i_D = i_S = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_t)^2$$

with Early Voltage:

$$\lambda = \frac{1}{V_A} \text{ where } V_A \neq \infty$$


$$i_D = i_S = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda |V_{DS}|)$$

Cutoff Region $|V_{GS}| < |V_t|$

$$i_D = i_G = i_S = 0$$

Large Signal Model

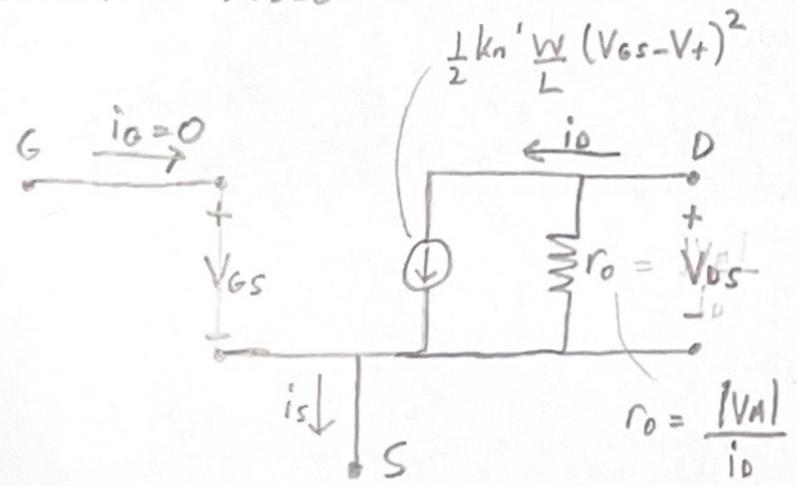* Enhancement N-MOSFET in Saturation mode




AC and DC Analysis

AC small signal model

Steps:

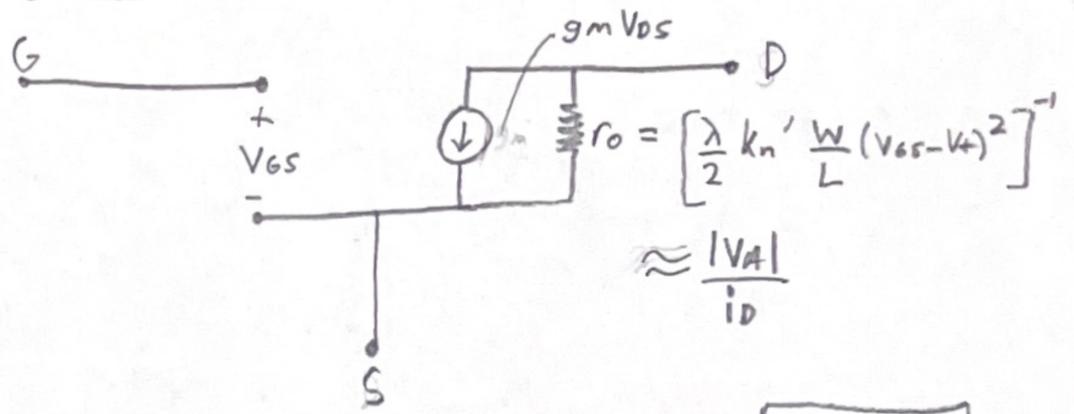- 1 Replace with DC circuit
- 2 Solve DC circuit for V_{GS} , i_D , V_{DS} . Make sure the MOSFET is in saturation
- 3 Replace with AC small signal model
- 4 Solve for voltage gain / current gain / etc




Formulas

$$\lambda = \frac{1}{V_A}$$


$$g_m = g_{m0} = k_n' \frac{W}{L} (V_{GS} - V_t)$$

Ideal Transformers

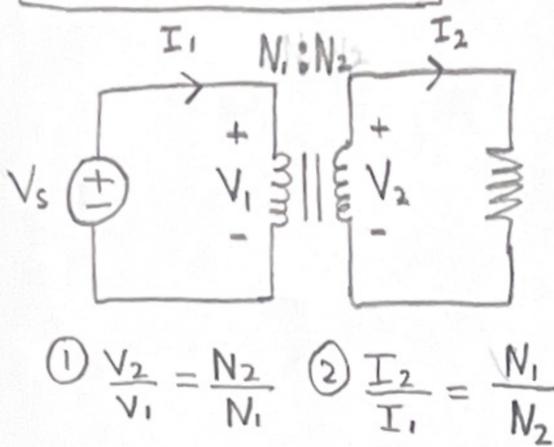

***Note:**
 $N_1 : N_2$
 \downarrow
 $1 : n$ $n = \frac{N_2}{N_1}$

laplace_transforms.png (2072x1674)

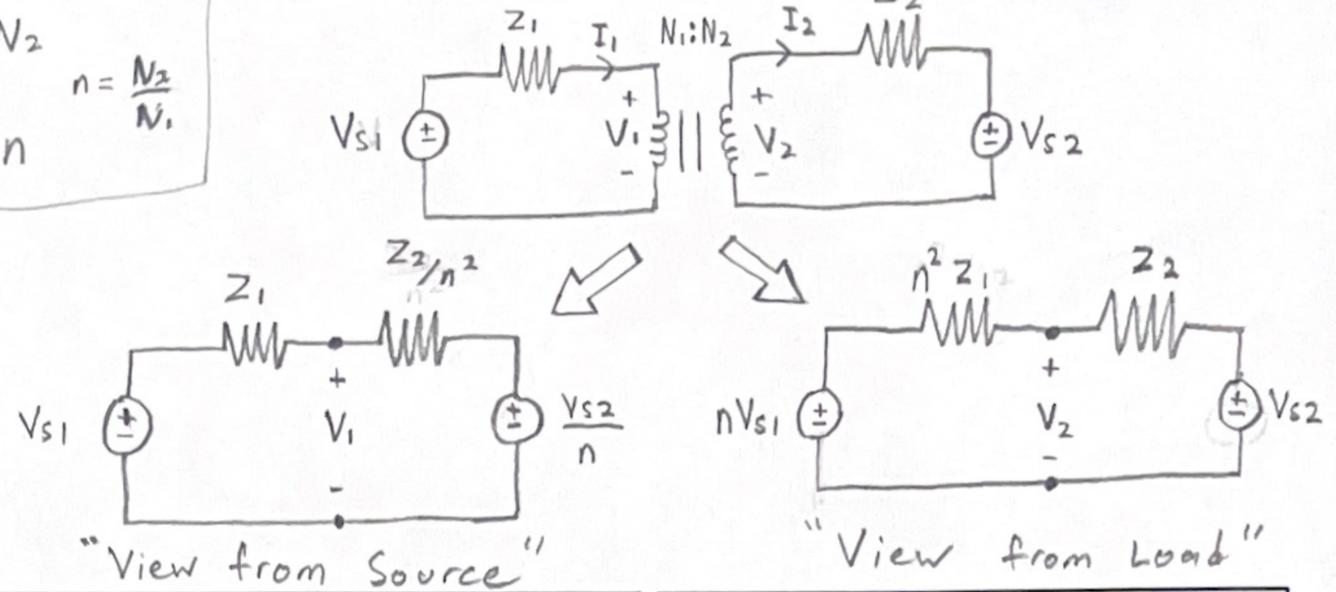

Laplace Tables

Property	$f(t)$	$F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F_1(s) + a_2F_2(s)$
Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time shift	$f(t-a)u(t-a)$	$e^{-as}F(s)$
Frequency shift	$e^{-at}f(t)$	$F(s+a)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2f}{dt^2}$	$s^2F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3f}{dt^3}$	$s^3F(s) - s^2f(0^-) - sf'(0^-) - f''(0^-)$
	$\frac{d^nf}{dt^n}$	$s^nF(s) - s^{n-1}f(0^-) - s^{n-2}f'(0^-) - \dots - f^{(n-1)}(0^-)$
Time integration	$\int_0^t f(t)dt$	$\frac{1}{s}F(s)$
Frequency differentiation	$tf(t)$	$-\frac{d}{ds}F(s)$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty F(s)ds$
Time periodicity	$f(t) = f(t+nT)$	$\frac{F_1(s)}{1 - e^{-sT}}$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$
t^n	$\frac{n!}{s^{n+1}}$
te^{-at}	$\frac{1}{(s+a)^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$\sin(\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
$\cos(\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$

*Defined for $t \geq 0$; $f(t) = 0$, for $t < 0$.

2nd Order Circuits

$s^2 + 2\alpha s + \omega_0^2 \longrightarrow \alpha > \omega_0$ OVERDAMPED

$\alpha = \omega_0$ CRITICALLY DAMPED


$\alpha < \omega_0$ UNDERDAMPED

① $i_L(0^+)$ and $V_C(0^+)$ found for $t < 0$ (long time)

② $i_L(0^+)$ and $V_C(0^+)$ found for $t > 0$ (after switch)

RMS Values

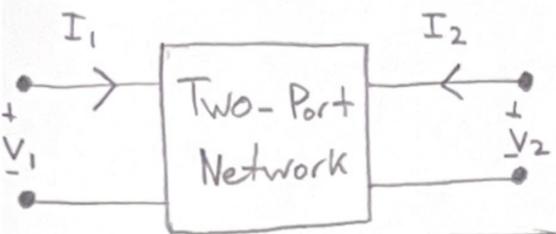$V_{rms} = \frac{1}{\sqrt{2}} V_p$ (Peak is bigger than rms)



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z \\ \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h \\ \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} T \\ \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} Y \\ \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g \\ \end{bmatrix} \begin{bmatrix} V_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} V_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} t \\ \end{bmatrix} \begin{bmatrix} V_1 \\ -i_1 \end{bmatrix}$$

Impedance Parameters:

Apply 1A to V1 side, Apply 1A to V2 side

$$V_1 = Z_{11}$$

$$V_2 = Z_{22}$$

$$V_2 = Z_{21}$$

$$V_1 = Z_{12}$$

TABLE 19.1

Conversion of two-port parameters.

	Impedance z	Admittance y	Hybrid h	Inverse Hybrid g	Transmission T	Inverse Transmission t
z	Z_{11}	Z_{12}	$\frac{Y_{22}}{\Delta_y}$	$-\frac{Y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$
	Z_{21}	Z_{22}	$-\frac{Y_{21}}{\Delta_y}$	$\frac{Y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$
y	$\frac{Z_{22}}{\Delta_z}$	$-\frac{Z_{12}}{\Delta_z}$	Y_{11}	Y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$
	$-\frac{Z_{21}}{\Delta_z}$	$\frac{Z_{11}}{\Delta_z}$	Y_{21}	Y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$
h	$\frac{\Delta_z}{Z_{22}}$	$\frac{Z_{12}}{Z_{22}}$	$\frac{1}{Y_{11}}$	$-\frac{Y_{12}}{Y_{11}}$	h_{11}	h_{12}
	$-\frac{Z_{21}}{Z_{22}}$	$\frac{1}{Z_{22}}$	$\frac{Y_{21}}{Y_{11}}$	$\frac{\Delta_y}{Y_{11}}$	h_{21}	h_{22}
g	$\frac{1}{Z_{11}}$	$-\frac{Z_{12}}{Z_{11}}$	$\frac{\Delta_y}{Y_{22}}$	$\frac{Y_{12}}{Y_{22}}$	$\frac{h_{22}}{\Delta_h}$	$-\frac{h_{12}}{\Delta_h}$
	$\frac{Z_{21}}{Z_{11}}$	$\frac{\Delta_z}{Z_{11}}$	$-\frac{Y_{21}}{Y_{22}}$	$\frac{1}{Y_{22}}$	$-\frac{h_{21}}{\Delta_h}$	$\frac{h_{11}}{\Delta_h}$
T	$\frac{Z_{11}}{Z_{21}}$	$\frac{\Delta_z}{Z_{21}}$	$-\frac{Y_{22}}{Y_{21}}$	$-\frac{1}{Y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$
	$\frac{1}{Z_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$-\frac{\Delta_y}{Y_{21}}$	$-\frac{Y_{11}}{Y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$
t	$\frac{Z_{22}}{Z_{12}}$	$\frac{\Delta_z}{Z_{12}}$	$-\frac{Y_{11}}{Y_{12}}$	$-\frac{1}{Y_{12}}$	$\frac{1}{h_{12}}$	$\frac{h_{11}}{h_{12}}$
	$\frac{1}{Z_{12}}$	$\frac{Z_{11}}{Z_{12}}$	$-\frac{\Delta_y}{Y_{12}}$	$-\frac{Y_{22}}{Y_{12}}$	$\frac{h_{22}}{h_{12}}$	$\frac{\Delta_h}{h_{12}}$


$$\Delta_z = Z_{11}Z_{22} - Z_{12}Z_{21}, \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21}, \quad \Delta_T = AD - BC$$

$$\Delta_y = Y_{11}Y_{22} - Y_{12}Y_{21}, \quad \Delta_g = g_{11}g_{22} - g_{12}g_{21}, \quad \Delta_t = ad - bc$$

Combining networks

- ① Series, impedances add
- ② Parallel, Admittances add
- ③ Cascade, Transmissions multiply


Model

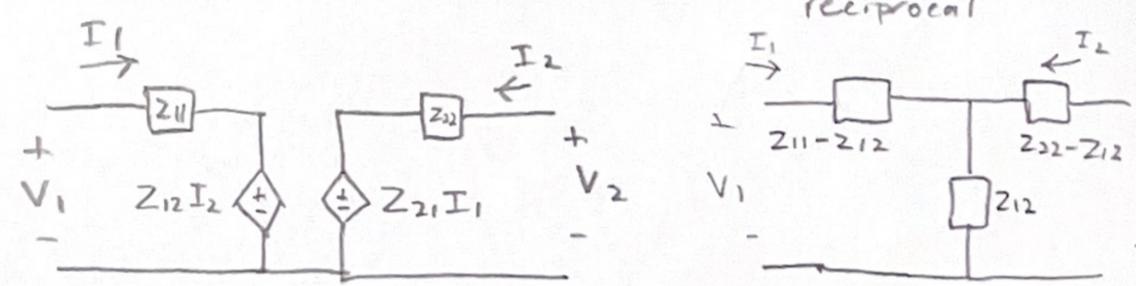

*if $Z_{12} = Z_{21}$ reciprocal


4 Types

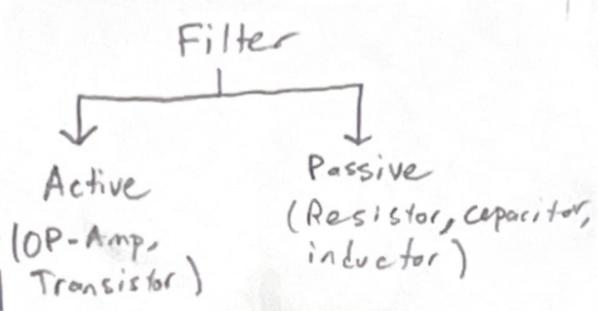- ① LOW-PASS
- ② HIGH-PASS
- ③ BAND-PASS
- ④ BAND-STOP




LOW-PASS Filter


RC LOW-PASS :

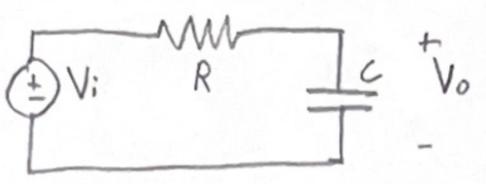


RL Low Pass

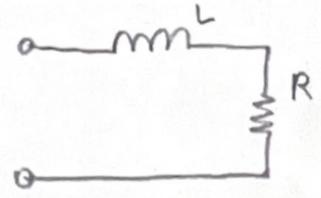

RL High Pass

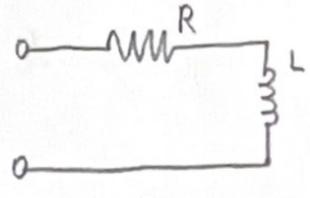

RC High Pass

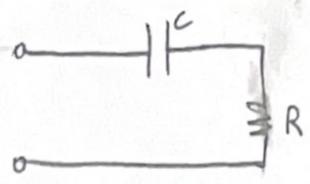

RLC Filter

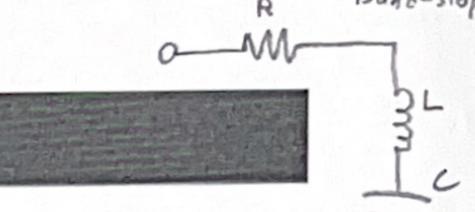
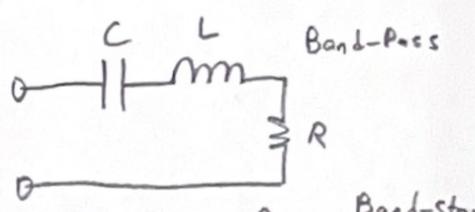
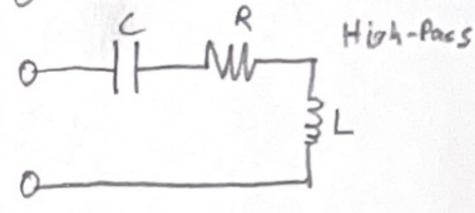
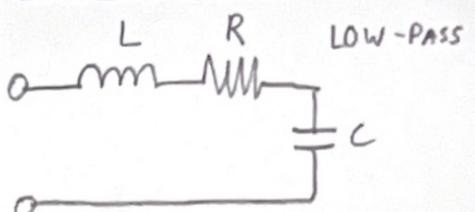


TABLE 14.4

Summary of the characteristics of resonant RLC circuits.

Characteristic	Series circuit	Parallel circuit
Resonant frequency, ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
(Flipped) Quality factor, Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
Bandwidth, B <small>$\omega_2, \omega_1 = \text{Poles of } H(s)$ $\omega_0 = \sqrt{\omega_1 \cdot \omega_2}$ $BW = \omega_2 - \omega_1$</small>	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
Half-power frequencies, ω_1, ω_2 <small>$BW = \omega_2 - \omega_1$</small>	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
For $Q \geq 10, \omega_1, \omega_2$	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

Scaling

$k_f = \frac{f_{new}}{f_{old}}$ fold

$L' = \frac{L_{old}}{k_f}$

$C' = \frac{k_f}{C_{old}}$

(Want to scale up components)

$R' = k_m \cdot R$

$L' = k_m \cdot L$

$C' = \frac{C}{k_m}$

(Change both) (General)

$R' = k_m \cdot R$

$L' = \frac{k_m}{k_f} \cdot L$

$C' = \frac{1}{k_m \cdot k_f} \cdot C$

